

Reg. No.: 21BCE1E96

Name : Vishal

**VIT[®]**

Vellore Institute of Technology

(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test I – September 2022

Programme	: B.Tech ECE/ECM	Semester	: FS 2022-23
Course	: Digital System Design	Code	: BECE102L
Faculty	: Dr.E.Manikandan	Class Nbr	: CH2022231001853
Time	: 90 Minutes	Slot	: E1+TE1
		Max. Marks	: 50

Answer ALL the questions

Q.No.	Sub-division	Question Text	Marks
1.		<p>a) Reduce the following Boolean expressions $WXY'Z + W'XZ + WXYZ$</p> <p>b) Express the given function as in a) in POS form</p>	[2] + [3]
2.		<p>$F(A,B,C,D) = \pi(1,4,6,12,14)$</p> <p>i) Simplify the given Boolean function in SOP form using K-Map. ii) Draw a CMOS logic circuit for this simplified expression. (Assume both true and complementary inputs are available)</p>	[5] + [5]
3.		Consider the combinational circuit shown	[5]
		Determine the truth table for the output F as a function of the four inputs.	
4.		<p>Simplify the given function and for the simplified expression write the Verilog program using (a) Behavioral and (b) dataflow modelling.</p> $F1 = \sum (1,2,3,6,8,9,10,12,13,14).$	[10]
5.		Identify the errors in the Verilog program given below for the Boolean expression $F = (A + \underline{CD})(\underline{A} + B)$.	
		<p>Module test (a, b, c, d, F)</p> <pre>input a,b,c,d; output F;</pre>	[10]

```

reg f1,f2,f3,f4;
not g1(f1,a);
nand g2(f2,c,d);
or g3(f1,f3,b);
or g3(f4,a,f2);
nand (F,f3,f4)
end module

```

Check for both syntactic and logical errors, Correct it.

6.


Design a full-subtractor circuit and implement the same

- using a suitable decoder.
- using NAND only

[10]

Total Marks

[50]

 

$$\bar{A}B + A\bar{B}$$

$$\bar{A}\cdot \bar{B}$$